
 


الجمهورية الجزائرية الديمقراطية الشعبية People's Democratic Republic of Algeria		
Ministry of Higher Education and Scientific Research National School of Cyber Security	 المدرسة الوطنية العليا في الأمن السيبراني NATIONAL SCHOOL OF CYBERSECURITY	وزارة التعليم العالي والبحث العلمي المدرسة الوطنية العليا في الأمن السيبراني
Foundation Training Department		قسم التكوين القاعدي
LEVEL : 1st Year Basic Training	Tutorial Sheet No. 6	MODULE : Computer Architecture1

Exercise 1.


For the input sequence in the below figure, draw the output waveform of:

- a negative edge-triggered JK flip-flop,
- a positive edge-triggered JK flip-flop.



 Exercise 2:

Consider the diagram in the figure below:



Given that:

- In addition to the JK inputs and the clock input H, the JK flip-flop has a Reset input that is active low and has priority over all other inputs.
 - As soon as Reset=0, Q=0.
- For what values of X and Y are the flip-flops reset to 0?
 - By drawing the timing diagram of the flip-flops QA, QB, QC, and QD, show that when QA=HB (where QA and HB are connected together), the circuit functions as a modulo-16 counter.
 - We need to design an asynchronous modulo-9 counter using JK flip-flops. Provide the corresponding circuit diagram.

Exercise 3:

Design a finite state machine that detects the sequence 1011 in a binary stream.

- Draw the state diagram.
- Provide the state transition table.

- Implement the machine using D flip-flops and logic gates.

Exercise 4:

- Design a 4-bit shift register that shifts data to the right with each clock pulse.
- Modify the shift register to include a parallel load feature.
- Describe its operation and draw the diagram.

Exercise 5:

Design a 4-bit universal shift register capable of the following operations:

- Shift left.
 - Shift right.
 - Parallel load.
 - Hold.
1. Draw the circuit diagram.
 2. Explain the control logic for selecting operations.

Exercise 6:

Design a 4-bit counter that can count both up and down depending on a control signal UP.

- Write the state table.
- Use JK flip-flops to implement the design.
- Simulate its behavior for UP=1 and UP=0.

Exercise 7:

1. Design a 4-bit **ring counter** using D flip-flops.
2. Initialize the counter with 1000.
3. Explain its operation and draw the timing diagram for four clock cycles.
4. Repeat the three first questions for the **johnson counter**