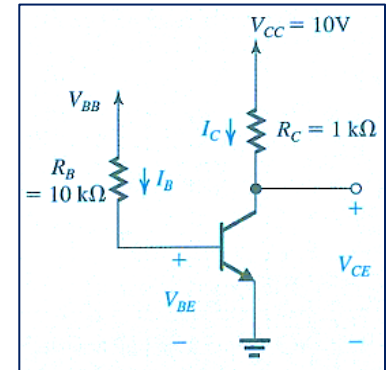


## Tutorial Work of Chapter 2: Bipolar Junction Transistor

### Exercise N°1


For a circuit shown in Figure, we need the value of  $V_{BB}$  for the transistor to operate in:

- 1- In the active mode with  $V_{ce} = 5V$ .
- 2- At the edge of saturation.
- 3- Deep in saturation with  $\beta_{forced} = 10$



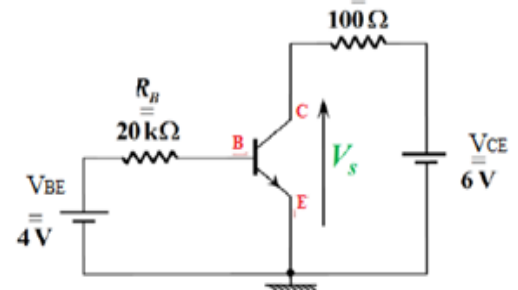
### Exercise N°2 :

Determine the currents  $I_B$  and  $I_C$  and the voltages  $V_S$  and  $V_{CB}$  in the transistor circuit shown in figure. Assume that the transistor operates in active mode and that the current gain is equal 50.


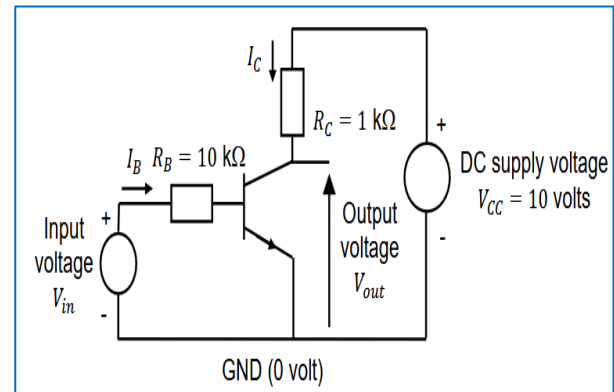
### Exercise N°3


Consider the circuit depicted below. The NPN BJT has a forward current gain  $\beta_F = 100$ . Find the DC voltage transfer characteristic for this circuit. In other words, for each value of the input voltage  $V_{in}$  ranging from 0 to  $V_{CC} = 10$  volts, we want to determine the corresponding output voltage  $V_{out}$ .


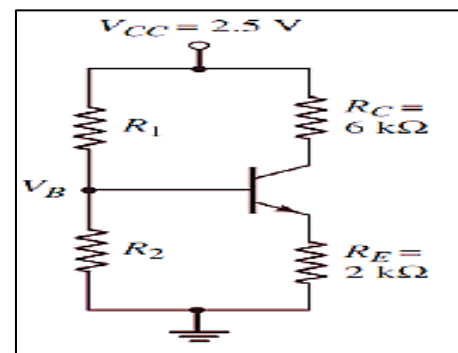
### Exercise N°4

For the transistor in the adjacent diagram, assume  $\beta = 120$ .

- 1- Identify the circuit elements so that:  $I_{CQ} = 0.15mA$  and  $R_{Th} = 200k\Omega$ .
- 2- Calculate the value of  $V_{CEQ}$ .




### Exercise N°5

#### Q-point

The operating point  $Q(8V, 5mA)$  is in the middle of the DC load line.

Calculate:  $V_{CC}$ ,  $R_B$  and  $R_E$

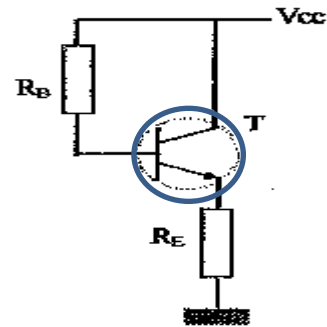**Given:**  $V_{BE} = 0.5V$  and  $\beta = 100$



### Exercise N°6


Consider the circuit shown in the figure where:

$V_{CC} = 5V$ ,  $\beta = 120$ ;  $V_{BE} = 0.7V$ ,  $V_{CEsat} = 0.2V$ ,  $R_B = 150K\Omega$  and  $R_C = 5K\Omega$ .  $V_{BB}$  can take values from 0V to 5V

1- Determine the value of  $V_{BB}$  at which the transistor switches from blocking to active operation. Find the values of the transistor currents and voltages for  $V_{BB} = 1.5V$ .


2- Determine the value of  $V_{BB}$  at which the transistor enters in the saturation state. Find the values of the transistor currents and voltages for  $V_{BB}=3V$  and calculate the value of the current gain.

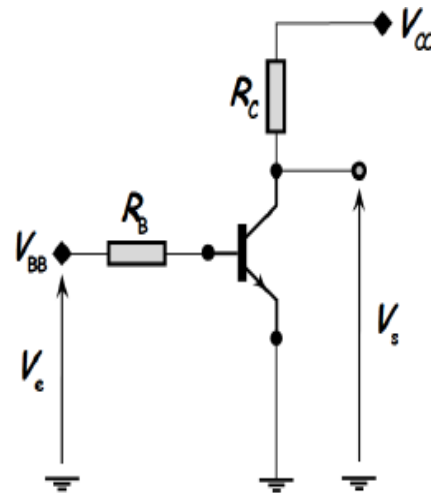3- Draw the graph  $I_C = f(V_{BB})$  and the voltage transfer characteristic  $V_s = f(V_e)$ .


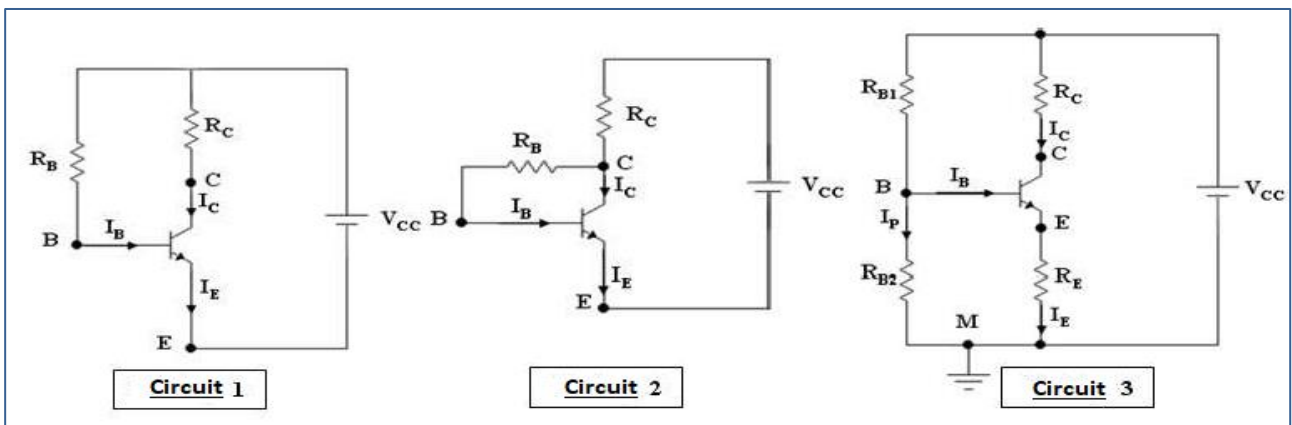
### Exercise N° 7

A silicon NPN transistor is used in the following three circuits:



- 1- Give the names of biasing methods expressed by its circuits.
- 2- Calculate the necessary polarization elements. For each circuit, the operating point (polarization) must be as follows:  $V_{CE0} = 5V$ ,  $I_{C0} = 1mA$ ,  $V_{CC} = 10V$ ,  $\beta = 100$  and  $V_{BE0} = 0.7V$ . For the circuit 3, we set  $I_p = 100\mu A$  and  $R_E = 1k\Omega$ .

### Exercise N°8


Consider the circuit shown in the following figure:

1- Calculate the silent points (Quiescent point: Q-point) ( $I_B$ ,  $I_C$  and  $V_{CE}$ ).

2- Express and plot the straight lines:  $I_C = f(V_{CE})$  and  $I_B = f(V_{BE})$ .

3- Represent the Q-points on their straight lines.

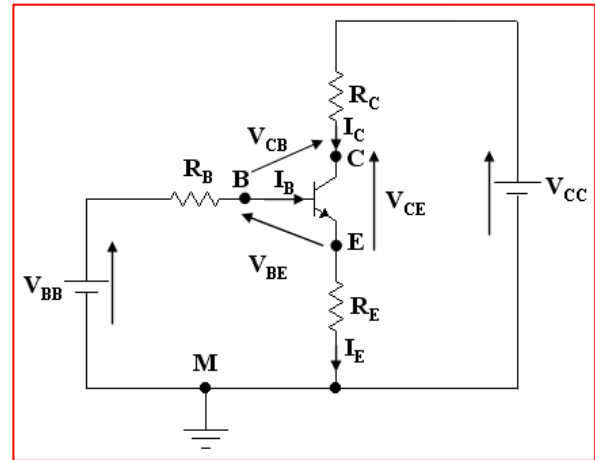Given:  $\beta=180$ ,  $V_{BB} = 5\text{ V}$ ,  $V_{CC} = 10\text{ V}$ ,  $V_{BE} = 0.6\text{ V}$ ,  $R_B = 10\text{ k}\Omega$ ,  $R_C = R_E = 100\text{ }\Omega$ .



### Exercise N°9

The transistor, in the circuit shown opposite, is defined by its characteristics given on the attached plot sheet.

We give:  $V_{CC} = 18\text{ V}$ ,  $R_1 = 268.2\text{ k}\Omega$ ,  $R_2 = 22.62\text{ k}\Omega$ ,  $R_C = 5.86\text{ k}\Omega$ , and  $R_E = 140\text{ }\Omega$ .


1/ Find graphically the static current gain,  $\beta$ , of the transistor.

2/ Determine the equation of the static drive line.

3/ Plot the static drive line on the input characteristic of the transistor. Deduce  $I_{BQ}$  and  $V_{BEQ}$  (coordinates of the input operating point  $Q_E$ ).

4/ Find the equation of the static load line.

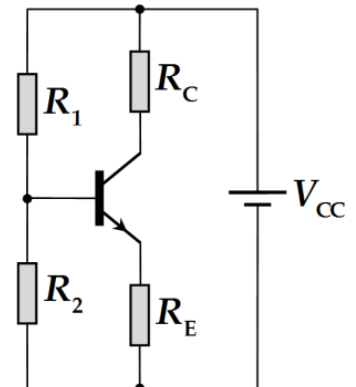5/ Plot the static load line on the transistor output characteristics. Deduce  $I_{CQ}$  and  $V_{CEQ}$  (coordinates of the output operating point Q).



### Exercise N°10

Consider the circuit shown in the figure opposite with :

$V_{CC} = 11\text{ V}$ ,  $R_C = 2.7\text{ k}\Omega$ ,  $R_E = 390\text{ }\Omega$ ,  $\beta = 135$ ,  $h_{11} = 2.7\text{ k}\Omega$ ,  $h_{12} = h_{21} = 0$ .

#### □ Static analysis:

Given  $V_{BE} = 0.7\text{ V}$  and  $V_C = 5.6\text{ V}$  (voltage between the collector and the ground).

a/ Find the value of  $R_B$ .


b/ Calculate the values of  $I_{CQ}$  and  $V_{CEQ}$ .

#### □ Dynamic analysis:

a/ Draw the equivalent circuit diagram.

b/ Find the input resistance.

c/ Determine the

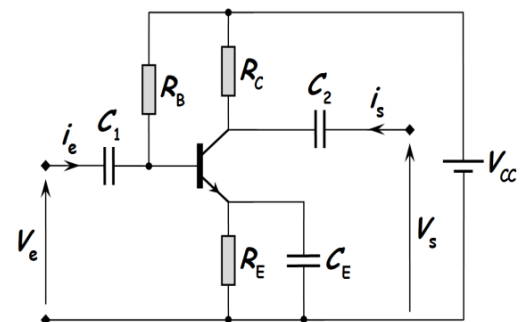


voltage gain.

### Exercise N°11

Let's consider the amplifier as in the figure on the right.

Where:  $I_C = I_E = 2.8\text{mA}$ ,  $V_{BE} = 0.6\text{V}$ ,  $V_{CC} = 24\text{V}$ ,  $h_{11} \ll R_1 // R_2$ ,  $h_{12} = h_{22} = 0$ ,  $h_{21} = \beta = 100$ .

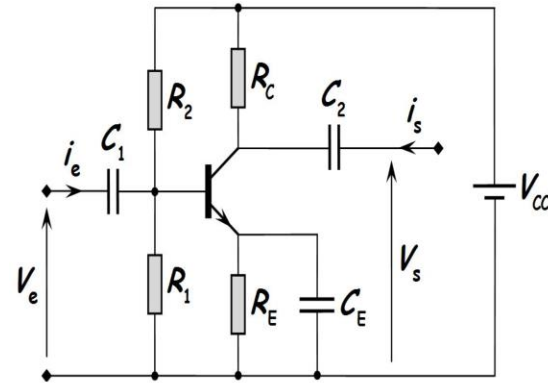1. Given that the amplifier has a no-load voltage gain of -220, an input impedance of  $900\ \Omega$ , and an operating point in the middle of the static load line, calculate the values of the resistors  $R_C$  and  $R_E$ .
2. Find  $R_1$  and  $R_2$  if  $R_B = 10R_E$  where  $R_B = R_1 // R_2$ .
3. An  $R_L$  load is placed between the collector and the ground at the output of the circuit.
  - a. Determine the gain in current.
  - b. Determine the output resistance.



### Exercise N°12

In this circuit  $h_{11} = 100\Omega$ ,  $\beta = 150$ ,  $h_{22}^{-1}$  infinite

Operating point  $V_{CE} = 7.5\text{V}$ ,  $I_C = 75\text{mA}$ ,  $V_{BE} = 700\text{mV}$

#### 1- Static study (DC study)

For  $V_{CC} = 15\text{V}$

- 1- What type of amplifier is it?
- 2- Give the role of the elements ( $R_1$ ,  $R_2$ ,  $R_E$ ,  $C_1$ ,  $C_2$ ,  $V_{CC}$ )
- 3- Calculate  $R_E$
- 4- Calculate  $R_1$  and  $R_2$  knowing that  $I_0 = 10 \cdot I_B$

#### 2- Dynamic study (for medium frequencies)

- 5- Draw the equivalent circuit diagram for an alternating signal
- 6- Calculate the voltage amplification  $A_v = V_2/V_1$  ( $R_{ch} = 100\Omega$ )
- 7- Calculate  $R_e$  (input resistance) between B and M and between the terminals of  $V_1$
- 8- Calculate the current amplification  $A_i = i_2/i_1$

