





Counters



Counters

- Counters are a specific type of sequential circuit.
- Like registers, the state, or the flip-flop values themselves, serves as the "output."
- The output value increases by one on each clock cycle.
- After the largest value, the output "wraps around" back to 0.
- Using two bits, we'd get something like this:

| Present State | | Next State | |
|---------------|---|------------|---|
| A | B | A | B |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

  

Benefits of counters

- Counters can act as simple clocks to keep track of "time."
- You may need to record how many times something has happened.
 - How many bits have been sent or received?
 - How many steps have been performed in some computation?
- All processors contain a **program counter**, or **PC**.
 - Programs consist of a list of instructions that are to be executed one after another (for the most part).
 - The PC keeps track of the instruction currently being executed.
 - The PC increments once on each clock cycle, and the next program instruction is then executed.

A slightly fancier counter

- Let's try to design a slightly different two-bit counter:
 - Again, the counter outputs will be 00, 01, 10 and 11.
 - Now, there is a single input, X . When $X=0$, the counter value should *increment* on each clock cycle. But when $X=1$, the value should *decrement* on successive cycles.
- We'll need two flip-flops again. Here are the four possible states:

00


01

11

10

The complete state diagram and table

 - Here's the complete state diagram and state table for this circuit.



| Present State | | Inputs X | Next State | |
|----------------|----------------|-------------|----------------|----------------|
| Q ₁ | Q ₀ | | Q ₁ | Q ₀ |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

D flip-flop inputs

- If we use D flip-flops, then the D inputs will just be the same as the desired next states.
- Equations for the D flip-flop inputs are shown at the right.
- Why does $D_0 = Q_0'$ make sense?

| Present State | | Inputs X | Next State | |
|---------------|-------|-------------|------------|-------|
| Q_1 | Q_0 | | Q_1 | Q_0 |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

| | | | | |
|-------|--|--|-------|---|
| | | | Q_0 | |
| | | | 0 | 1 |
| | | | 1 | 0 |
| | | | X | |
| Q_1 | | | | |


$$D_1 = Q_1 \oplus Q_0 \oplus X$$

| | | | | |
|-------|--|--|-------|---|
| | | | Q_0 | |
| | | | 1 | 0 |
| | | | 1 | 0 |
| | | | X | |
| Q_1 | | | | |

$$D_0 = Q_0'$$

The counter in LogicWorks

- Here are some **D Flip Flop** devices from LogicWorks.
- They have both normal and complemented outputs, so we can access $Q0'$ directly without using an inverter. ($Q1'$ is not needed in this example.)
- This circuit counts normally when **Reset** = 1. But when Reset is 0, the flip-flop outputs are cleared to 00 immediately.
- There is no three-input XOR gate in LogicWorks so we've used a four-input version instead, with one of the inputs connected to 0.

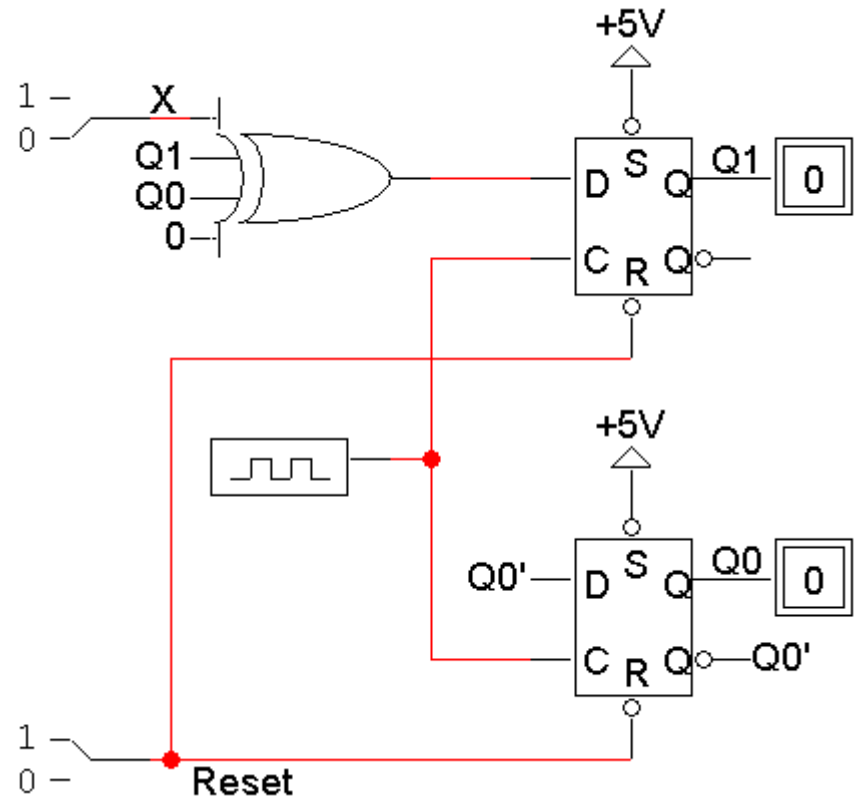

JK flip-flop inputs

- If we use JK flip-flops instead, then we have to compute the JK inputs for each flip-flop.
- Look at the present and desired next state, and use the excitation table on the right.

| Q(t) | Q(t+1) | J | K |
|------|--------|---|---|
| 0 | 0 | 0 | x |
| 0 | 1 | 1 | x |
| 1 | 0 | x | 1 |
| 1 | 1 | x | 0 |

| Present State | | Inputs | Next State | | Flip flop inputs | | | |
|----------------|----------------|--------|----------------|----------------|------------------|----------------|----------------|----------------|
| Q ₁ | Q ₀ | X | Q ₁ | Q ₀ | J ₁ | K ₁ | J ₀ | K ₀ |
| 0 | 0 | 0 | 0 | 1 | 0 | x | 1 | x |
| 0 | 0 | 1 | 1 | 1 | 1 | x | 1 | x |
| 0 | 1 | 0 | 1 | 0 | 1 | x | x | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | x | x | 1 |
| 1 | 0 | 0 | 1 | 1 | x | 0 | 1 | x |
| 1 | 0 | 1 | 0 | 1 | x | 1 | 1 | x |
| 1 | 1 | 0 | 0 | 0 | x | 1 | x | 1 |
| 1 | 1 | 1 | 1 | 0 | x | 0 | x | 1 |

JK flip-flop input equations

| Present State | | Inputs | Next State | | Flip flop inputs | | | |
|---------------|-------|--------|------------|-------|------------------|-------|-------|-------|
| Q_1 | Q_0 | | Q_1 | Q_0 | J_1 | K_1 | J_0 | K_0 |
| 0 | 0 | 0 | 0 | 1 | 0 | x | 1 | x |
| 0 | 0 | 1 | 1 | 1 | 1 | x | 1 | x |
| 0 | 1 | 0 | 1 | 0 | 1 | x | x | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | x | x | 1 |
| 1 | 0 | 0 | 1 | 1 | x | 0 | 1 | x |
| 1 | 0 | 1 | 0 | 1 | x | 1 | 1 | x |
| 1 | 1 | 0 | 0 | 0 | x | 1 | x | 1 |
| 1 | 1 | 1 | 1 | 0 | x | 0 | x | 1 |


- We can then find equations for all four flip-flop inputs, in terms of the present state and inputs. Here, it turns out $J_1 = K_1$ and $J_0 = K_0$.

$$J_1 = K_1 = Q_0' X + Q_0 X'$$

$$J_0 = K_0 = 1$$



The counter in LogicWorks again

 - Here is the counter again, but using **JK Flip Flop**.
- The direct inputs R and S are non-inverted, or active-high.
- So this version of the circuit counts normally when **Reset = 0**, but initializes to 00 when Reset is 1.




Asynchronous Counters

- This counter is called *asynchronous* because not all flip flops are hooked to the same clock.
- Look at the waveform of the output, Q , in the timing diagram. It resembles a clock as well. If the period of the clock is T , then what is the period of Q , the output of the flip flop? It's $2T$!
- We have a way to create a clock that runs twice as slow. We feed the clock into a T flip flop, where T is hardwired to 1. The output will be a clock whose period is twice as long.

  



Asynchronous counters

 If the clock has period T .
 Q_0 has period $2T$. Q_1
period is $4T$
With n flip flops the period
is 2^n .




3 bit asynchronous "ripple" counter using T flip flops

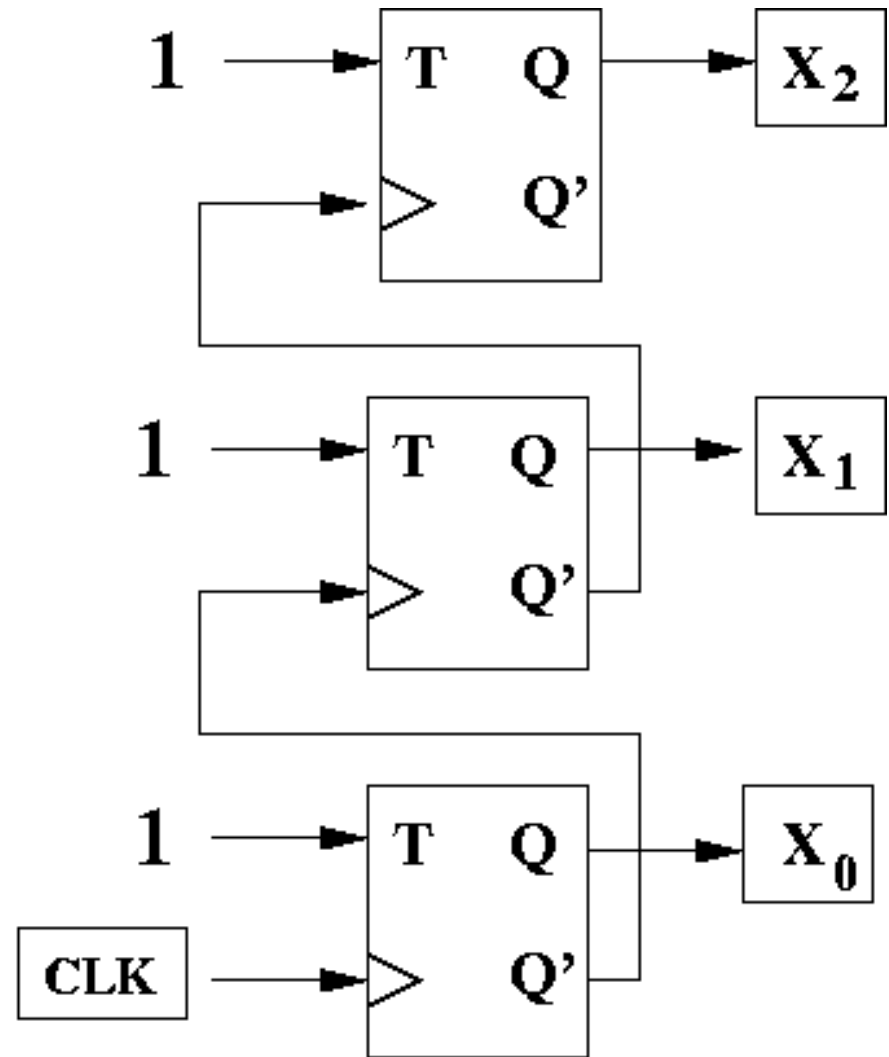 - This is called as a *ripple counter* due to the way the FFs respond one after another in a kind of rippling effect.




Synchronous Counters

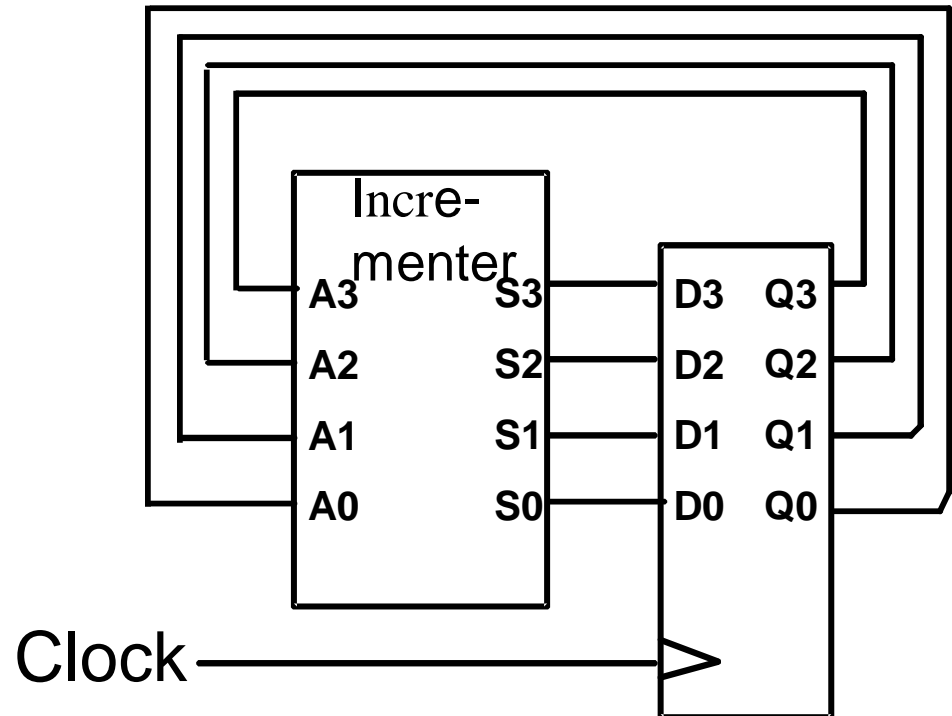- To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- For an up-counter, use an incrementer =>



Synchronous Counters (continued)

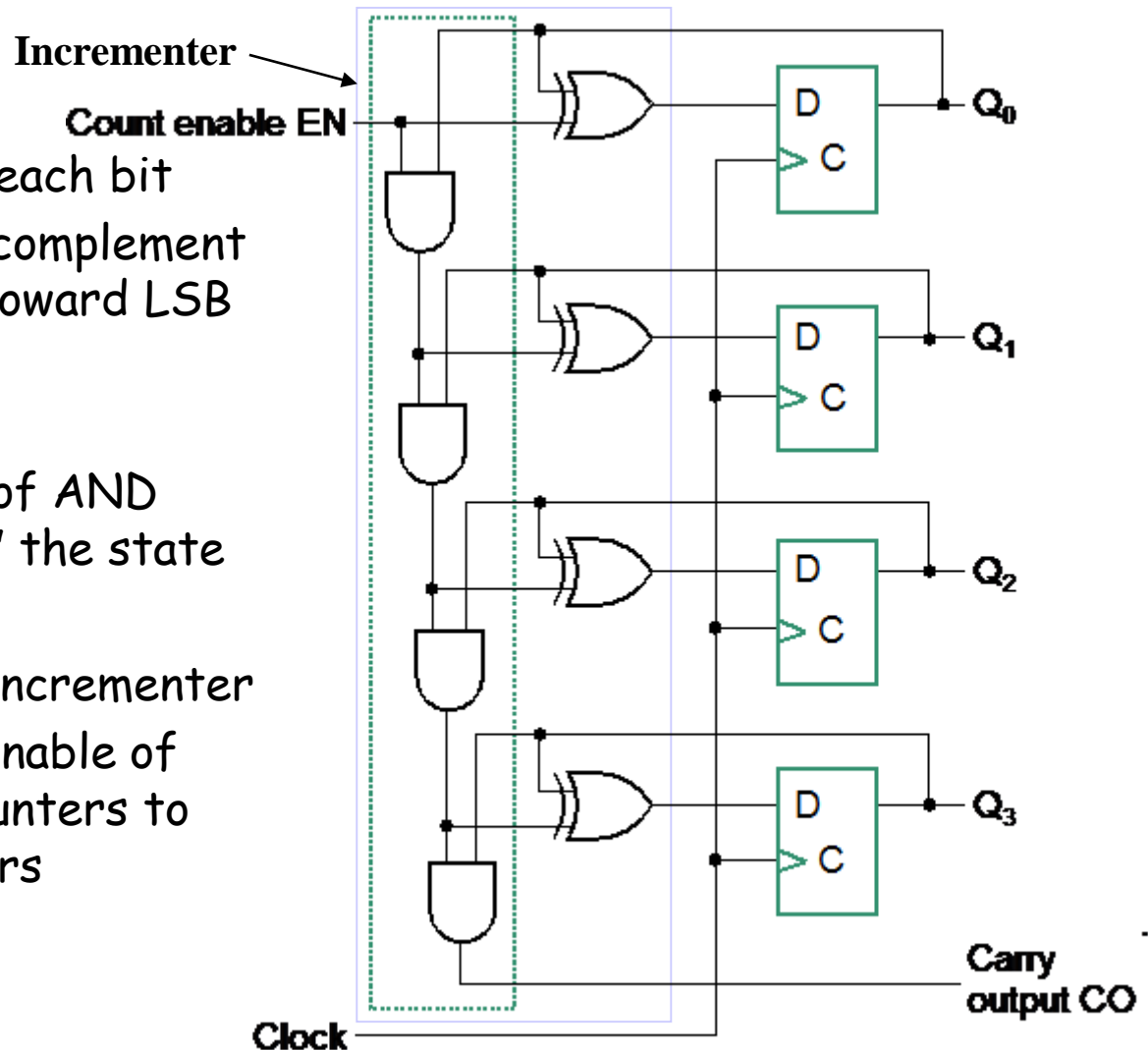- Internal details =>
- Internal Logic
 - XOR complements each bit
 - AND chain causes complement of a bit if all bits toward LSB from it equal 1
- Count Enable
 - Forces all outputs of AND chain to 0 to "hold" the state
- Carry Out
 - Added as part of incrementer
 - Connect to Count Enable of additional 4-bit counters to form larger counters



Design Example: Synchronous BCD

- Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- State Table =>
- Input combinations 1010 through 1111 are don't cares

| Current State Q8 Q4 Q2 Q1 | Next State Q8 Q4 Q2 Q1 |
|------------------------------|---------------------------|
| 0 0 0 0 | 0 0 0 1 |
| 0 0 0 1 | 0 0 1 0 |
| 0 0 1 0 | 0 0 1 1 |
| 0 0 1 1 | 0 1 0 0 |
| 0 1 0 0 | 0 1 0 1 |
| 0 1 0 1 | 0 1 1 0 |
| 0 1 1 0 | 0 1 1 1 |
| 0 1 1 1 | 1 0 0 0 |
| 1 0 0 0 | 1 0 0 1 |
| 1 0 0 1 | 0 0 0 0 |


Synchronous BCD (continued)

- Use K-Maps to two-level optimize the next state equations and manipulate into forms containing XOR gates:
 $D1 = Q1'$
- $D2 = Q2 \oplus Q1Q8'$
 $D4 = Q4 \oplus Q1Q2$
 $D8 = Q8 \oplus (Q1Q8 + Q1Q2Q4)$
 - $Y = Q1Q8$
- The logic diagram can be drawn from these equations
 - An asynchronous or synchronous reset should be added
- What happens if the counter is perturbed by a power disturbance or other interference and it enters a state other than 0000 through 1001?

Synchronous BCD (continued)

- Find the actual values of the six next states for the don't care combinations from the equations
- Find the overall state diagram to assess behavior for the don't care states (states in decimal)

| Present State | Next State |
|---------------|-------------|
| Q8 Q4 Q2 Q1 | Q8 Q4 Q2 Q1 |
| 1 0 1 0 | 1 0 1 1 |
| 1 0 1 1 | 0 1 1 0 |
| 1 1 0 0 | 1 1 0 1 |
| 1 1 0 1 | 0 1 0 0 |
| 1 1 1 0 | 1 1 1 1 |
| 1 1 1 1 | 0 0 1 0 |

 


Synchronous BCD (continued)

- For the BCD counter design, if an invalid state is entered, return to a valid state occurs within two clock cycles
- Is this adequate?!

Counting an arbitrary sequence

□ **TABLE 7-10**
State Table and Flip-Flop Inputs for Counter


| Present State | | | Next State | | |
|---------------|---|---|--------------------------------------|---|---|
| A | B | C | DA = DB = DC = A(t+1)B(t+1)C(t+1) | | |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |

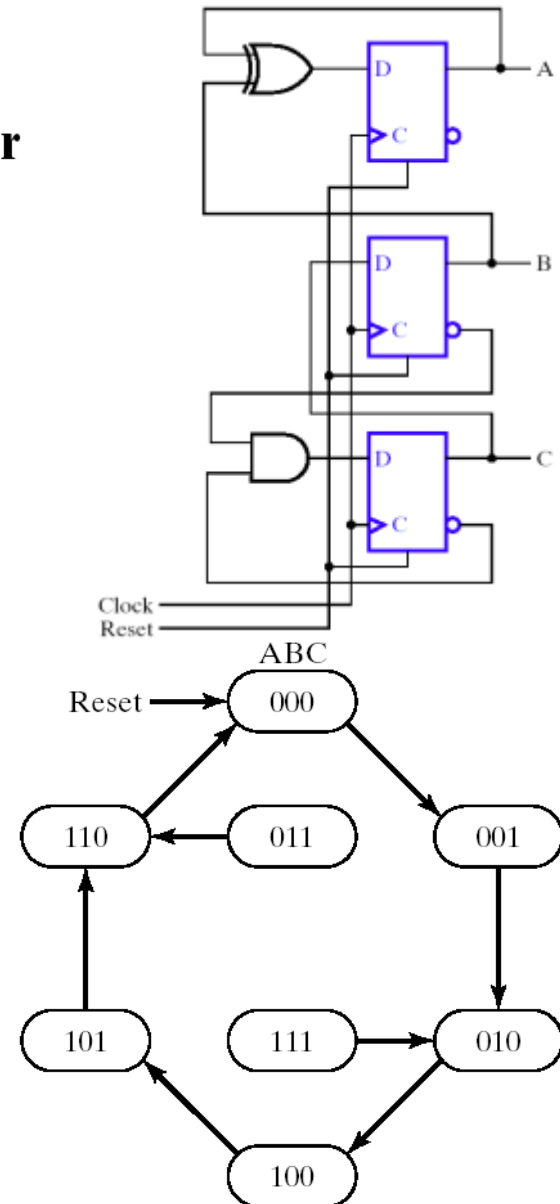

Unused states

- The examples shown so far have all had 2^n states, and used n flip-flops. But sometimes you may have unused, leftover states.
- For example, here is a state table and diagram for a counter that repeatedly counts from 0 (000) to 5 (101).
- What should we put in the table for the two unused states?


| Present State | | | Next State | | |
|---------------|-------|-------|------------|-------|-------|
| Q_2 | Q_1 | Q_0 | Q_2 | Q_1 | Q_0 |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | ? | ? | ? |
| 1 | 1 | 1 | ? | ? | ? |

 

Unused states can be don't cares...

- To get the *simplest* possible circuit, you can fill in don't cares for the next states. This will also result in don't cares for the flip-flop inputs, which can simplify the hardware.
- If the circuit somehow ends up in one of the unused states (110 or 111), its behavior will depend on exactly what the don't cares were filled in with.


| Present State | | | Next State | | |
|---------------|-------|-------|------------|-------|-------|
| Q_2 | Q_1 | Q_0 | Q_2 | Q_1 | Q_0 |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | x | x | x |
| 1 | 1 | 1 | x | x | x |

 

...or maybe you do care


- To get the *safest* possible circuit, you can explicitly fill in next states for the unused states 110 and 111.
- This guarantees that even if the circuit somehow enters an unused state, it will eventually end up in a valid state.
- This is called a **self-starting counter**.

| Present State | | | Next State | | |
|---------------|-------|-------|------------|-------|-------|
| Q_2 | Q_1 | Q_0 | Q_2 | Q_1 | Q_0 |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

 


LogicWorks counters

 - There are a couple of different counters available in LogicWorks.
- The simplest one, the **Counter-4 Min**, just increments once on each clock cycle.
 - This is a four-bit counter, with values ranging from 0000 to 1111.
 - The only "input" is the clock signal.



More complex counters


- More complex counters are also possible. The full-featured LogicWorks **Counter-4** device below has several functions.
 - It can increment or decrement, by setting the **UP** input to 1 or 0.
 - You can immediately (asynchronously) clear the counter to 0000 by setting **CLR** = 1.
 - You can specify the counter's next output by setting **D₃-D₀** to any four-bit value and clearing **LD**.
 - The active-low **EN** input enables or disables the counter.
 - When the counter is disabled, it continues to output the same value without incrementing, decrementing, loading, or clearing.
 - The "counter out" **CO** is normally 1, but becomes 0 when the counter reaches its maximum value, 1111.

 

-


A restricted 4-bit counter

 - We can also make a counter that "starts" at some value besides 0000.
- In the diagram below, when $CO=0$ the LD signal forces the next state to be loaded from D_3-D_0 .
- The result is this counter wraps from 1111 to 0110 (instead of 0000).



Another restricted counter

 - We can also make a circuit that counts up to only 1100, instead of 1111.
- Here, when the counter value reaches 1100, the NAND gate forces the counter to load, so the next state becomes 0000.



Summary of Counters

- Counters serve many purposes in sequential logic design.
- There are lots of variations on the basic counter.
 - Some can increment or decrement.
 - An enable signal can be added.
 - The counter's value may be explicitly set.
- There are also several ways to make counters.
 - You can follow the sequential design principles to build counters from scratch.
 - You could also modify or combine existing counter devices.

