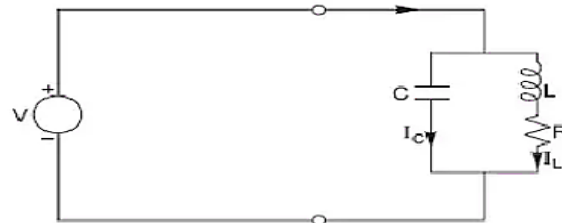


Tutorial Work of Chapter 3 : Electrical Circuit

Exercise N°1

Consider an RLC circuit supplied by a sinusoidal source and connected in parallel.





Given : $R=60\Omega$
 $L=200\text{mH}$
 $C=120\mu\text{F}$

- 1- Calculate the equivalent admittance of the circuit.
- 2- Determine the resonant frequency

Note: Parallel resonance occurs when the supply frequency creates zero phase difference between the supply voltage and current producing a resistive circuit

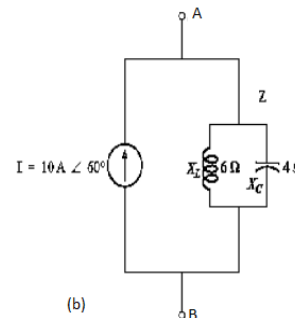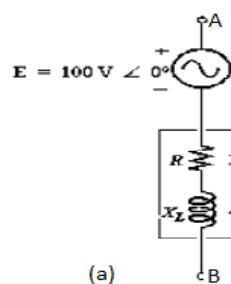
Exercise N°2

- 1- Convert the voltage source of Figure to a current source (fig a).
- 2- Convert the current source of Figure to a voltage source (fig b).



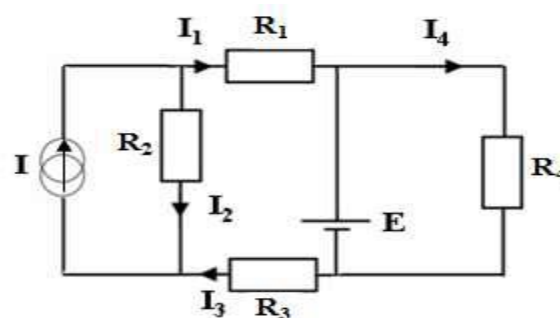Exercise N° 3


Consider the circuit shown in the figure below:




Determine the currents I_1 , I_2 , I_3 and I_4 , using the Superposition method.

Exercise N° 4


Use the superposition theorem to find I_0 in the figure shown.

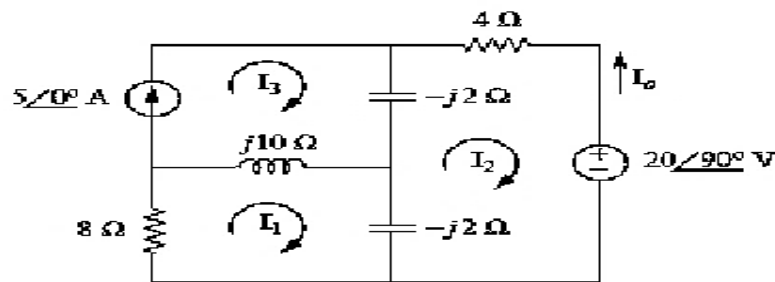**Exercise N°5**


Find I in the circuit of shown figure using superposition.

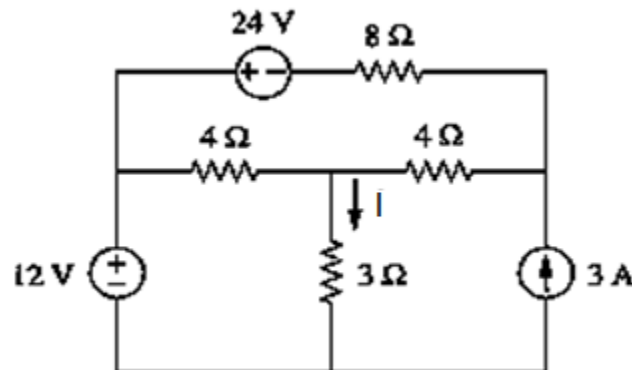**Exercise N°6**

Find the Thevenin equivalent circuit for the portion of the network to the left of terminal a-a' in Figure.

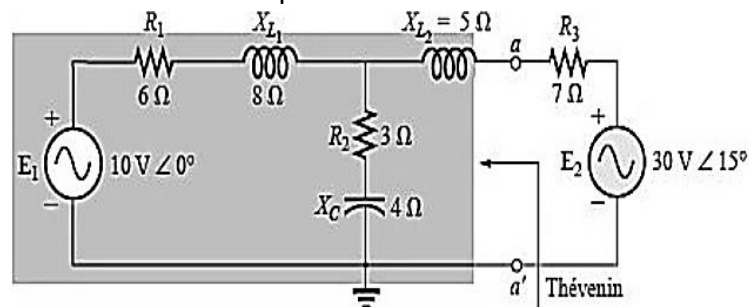**Exercise N°7**

Consider the following circuit:

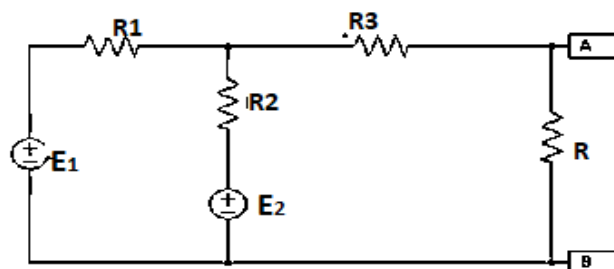


- 1- Find the equivalent Thevenin circuit as seen by terminals A and B
- 2- Calculate the value of the current flowing through resistance R and the voltage U across it.


Given: $E_1=240\text{ V}$, $E_2=180\text{ V}$, $R_1=24\Omega$, $R_2=16\Omega$, $R_3=6.4\Omega$ and $R=24\Omega$

Exercise N° 8

Obtain current I_o in Figure. using Norton's theorem

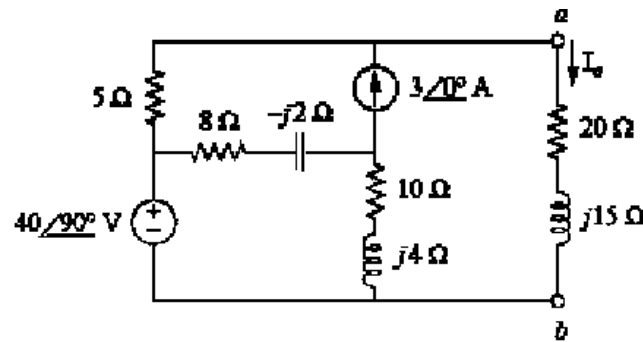**Exercise N°9**

Consider the following circuit:

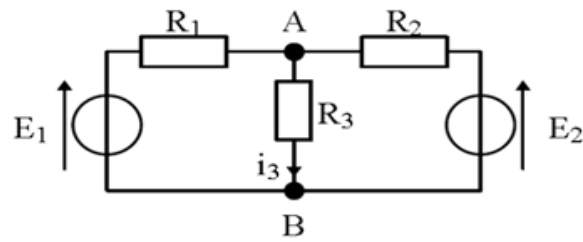

$$E_1 = 10 \text{ V}, E_2 = 5 \text{ V}, R_1 = 15 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega \text{ and } R_3 = 5 \text{ k}\Omega$$

- 1- Calculate the Norton equivalent Circuit of the AB dipole.
- 2- Deduce the value of i_3 .
- 3- Derive the Thévenin equivalent diagram of this dipole.