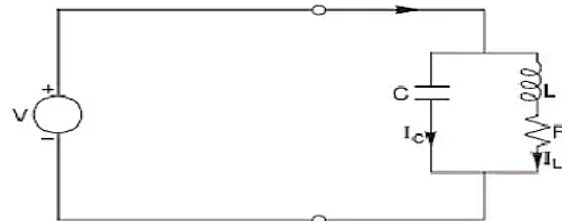


Tutoriel Work of Chapter 3: Electrical Circuit

Exercise N°1

Consider an RLC circuit supplied by a sinusoidal source and connected in parallel.







Given : $R=60\Omega$
 $L=200\text{mH}$
 $C=120\text{nF}$

- 1- Calculate the equivalent admittance of the circuit.
- 2- Determine the resonant frequency

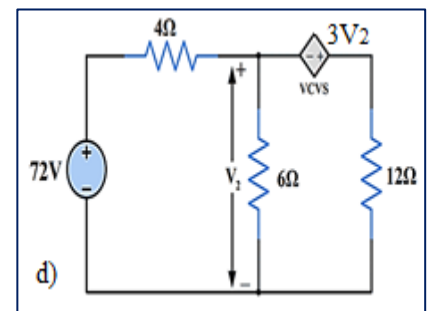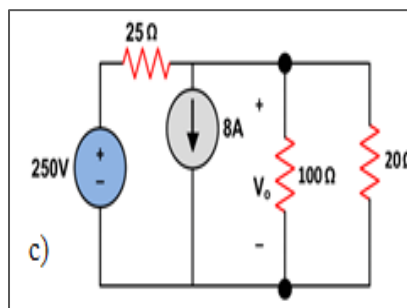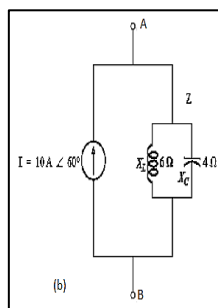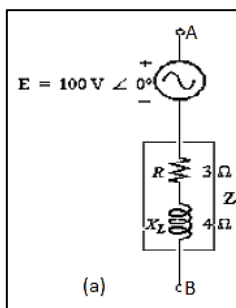
Exercise N°2

- 1- Convert the voltage source of Figure to a current source (fig a).
- 2- Convert the current source of Figure to a voltage source (fig b).
- 3- Find V_o using source Transformation (fig. c)
- 4- find v_2 in the following circuit using source transformation (fig.d).



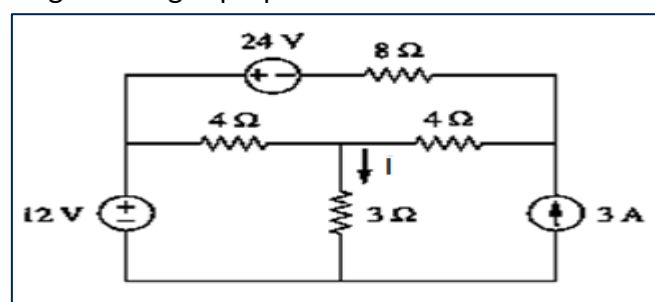
Exercise N° 3

Find I in the circuit of shown figure using superposition.



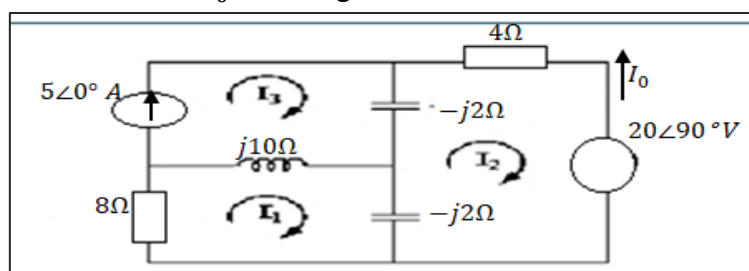
Exercise N°4

Use the superposition theorem to find I_0 in the figure shown.



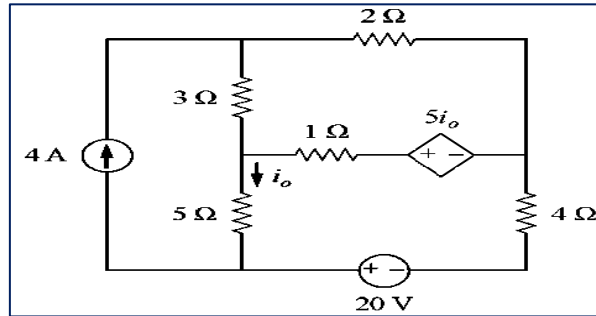
Exercise N°5:

For the following circuit, determine the current i_o using superposition.



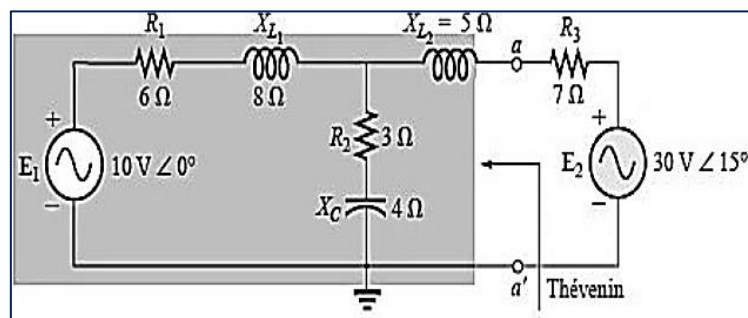
Exercise N°6

Find the Thevenin equivalent circuit for the portion of the network to the left of terminal a-a' in Figure.



Exercise N°7

Consider the following circuit:

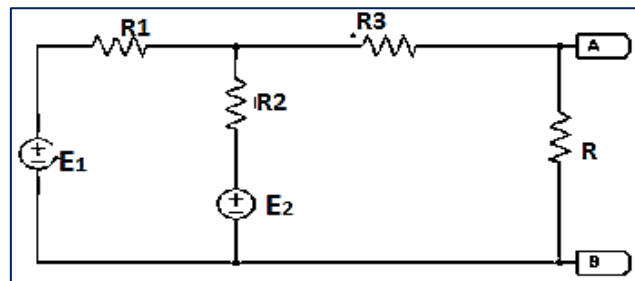


- 1- Find the equivalent Thévenin circuit as seen by terminals A and B
- 2- Calculate the value of the current flowing through resistance R and the voltage U across it.

Given: $E_1=240\text{ V}$, $E_2=180\text{ V}$, $R_1=24\Omega$, $R_2=16\Omega$, $R_3=6.4\Omega$ and $R=24\Omega$

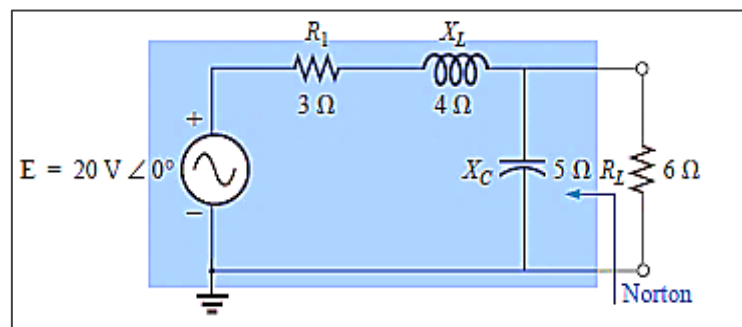
Exercise N° 8

Determine the Norton equivalent circuit for the network external to the 6Ω resistor –the load charge) of the following circuit



Exercise N°9

Consider the following circuit:

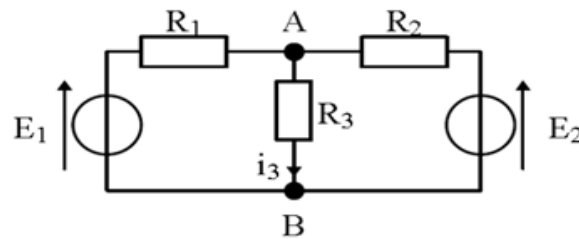


$$E_1 = 10 \text{ V}, E_2 = 5 \text{ V}, R_1 = 15 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega \text{ and } R_3 = 5 \text{ k}\Omega$$


- 1- Calculate the Norton equivalent Circuit of the AB dipole.
- 2- Deduce the value of i_3 .
- 3- Derive the Thévenin equivalent diagram of this dipole.

Exercise N°10

Using Millman's Theorem, find the current through the branch 'ab'

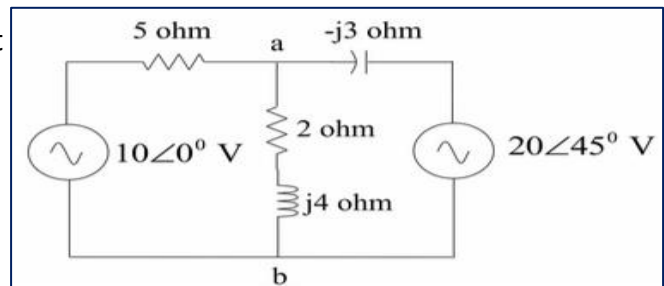**Exercise N°11**

Determine the d.d.p. V_{XY} , V_{R1} , V_{R2} and V_{R3} for the electrical circuit shown opposite:

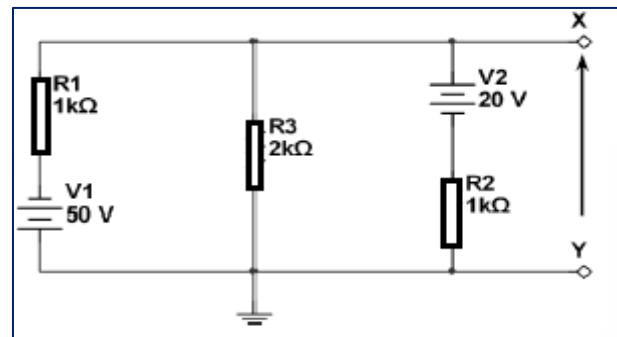**Exercise N°12**

- 1- Consider the following circuit:

Given: $R_1 = 10 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $r = 1 \text{ k}\Omega$
 $E_1 = 10 \text{ V}$ and $E_2 = 10 \text{ V}$

Using the Kenelly transform (triangle-star transform), find the current intensities: I , I_1 and I_2 .

- b- 2- Calculate the potentials V_B , V_A , V_C and V_H , taking point G as the reference point for the potential $V_G = 0$.

