

Tutorials series for chapter 1 : Direct Current Circuits: Basic concepts

Exercise N° 1

- 1- How much charge is represented by 4600 electrons?
- 2- The total charge entering a terminal is given by: $q(t) = 5t \sin(4\pi t) \text{ mC}$.
- 3- Determine the total charge entering a terminal between $t = 1 \text{ s}$ and $t = 2 \text{ s}$, if the current passing the terminal is $i(t) = (3t^2 - t) \text{ A}$

Exercise N°2

A metal wire is carrying an electric current, which is known to consist of electrons, such that the charge passing through any cross-section is given by the expression: $q(t) = -0.5t$, where $q(t)$ is expressed in coulombs.

- 1- What is the value of the current intensity $i(t)$?
- 2- What is the number of electrons that flow through a section of the wire each second?

Exercise N°3


- 1- A capacitor with a capacity of $100 \mu\text{F}$ must have an energy reserve of 50 Joules in order to operate a flash lamp.
 - a. What voltage is required to charge the capacitor?
 - b. What is the charge passing through the flash lamp?
- 2- A parallel-plate capacitor is made up of 5 cm square plates separated by a distance of 0.1 mm . Find its capacitance:
 - a. In air ($\epsilon = \epsilon_0$).
 - b. In a medium of $\epsilon = 6\epsilon_0$

Exercise N°4

Consider the circuit diagram below.


- 1- Knowing that capacitor C_1 carries charge $Q_1 = 10 \mu\text{C}$, what will be the potential difference V_{AD} between points A and D?
- 2- Determine the charges Q_2 and Q_3 of capacitors C_2 and C_3 respectively.
- 3- Given the potential difference between B and D equal to 2V, calculate the charges Q_4 and Q_5 of capacitors C_4 and C_5 .
- 4- What is the equivalent capacity C_{eq} of the entire circuit?

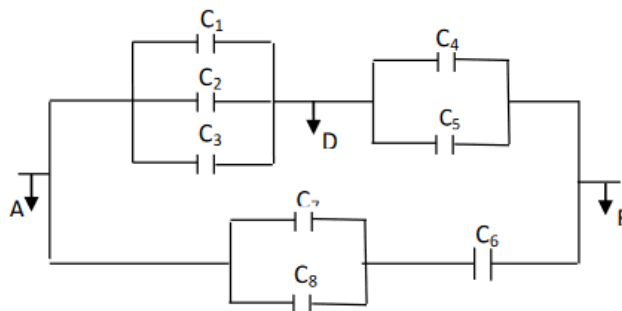We give : $C_1 = 4 \mu\text{F}$, $C_2 = 3.5 \mu\text{F}$, $C_3 = 2.5 \mu\text{F}$, $C_4 = C_5 = C_7 = C_8 = 5 \mu\text{F}$, $C_6 = 10 \mu\text{F}$



Exercise N°5


Calculate the charge and voltage across each of the capacitors when they are charged to their final voltage.

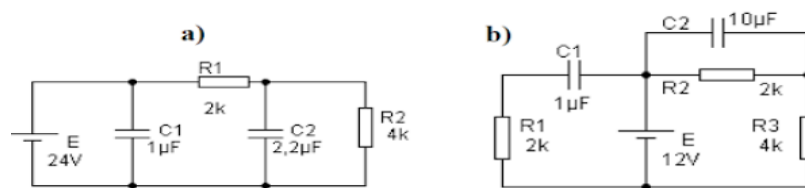**Exercise N°6**

We consider a parallel-plate capacitor, formed by two rectangular plates A and B of length L and width X . The two plates are separated by a distance of $2d$.

1. Calculate the charge accumulated by the capacitor when a voltage V is applied between the plates.
2. A metal plate of thickness $d/2$, initially neutral, is introduced between plates A and B (with the same dimensions). Represent qualitatively the new charge distribution on plates A, B, D, and E.
3. Calculate these charges.

Given: $L = 12 \text{ cm}$, $X = 10 \text{ cm}$, $d = 2 \text{ cm}$, $V = 400 \text{ V}$

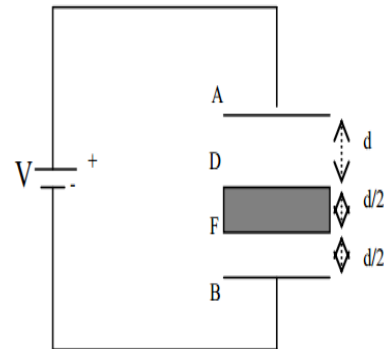**Exercise N° 7**

The following electrical circuit consists of two batteries (e_1, r_1) and (e_2, r_2), a galvanometer (G, r), two resistors R_1 , and R and a switch k .


k is closed:

1. Give the numbers of junction N , branches B and independent loop M .
2. Applying Kirchhoff's laws, calculate the currents flowing in each circuit branch.
3. Calculate the power supplied, consumed and lost in the circuit.
4. Deduce the Power efficiency



k is now open:

5. For what new value of electromotive force (e.m.f) e_2 does the G galvanometer display a current of zero current?

Given : $R_1 = 100\Omega$, $R = 200\Omega$, $e_1(12V, 2\Omega)$, $e_2(9V, 1\Omega)$.

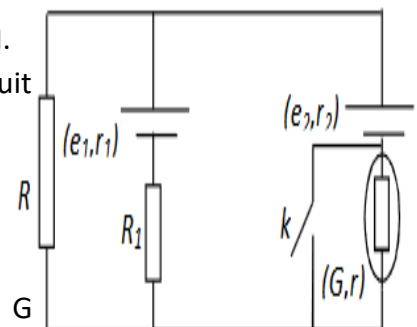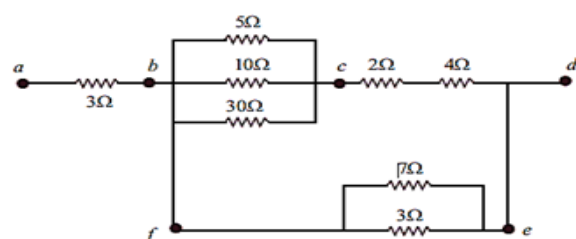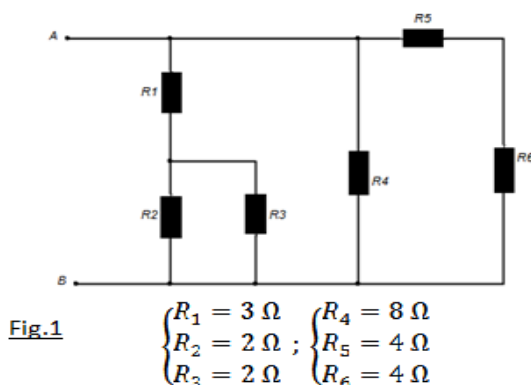**Exercise N°8**



Refer to the networks shown in Figure. Calculate the equivalent resistance



Exercise N°9 : Equivalent Resistance, Current, and Power in a Series Circuit

A battery with a terminal voltage of 9 V is connected to a circuit consisting of four 20Ω and one 10Ω resistors all in series (Figure 1). Assume the battery has negligible internal resistance

- Calculate the equivalent resistance of the circuit.
- Calculate the current through each resistor.
- Calculate the potential drop across each resistor.
- Determine the total power dissipated by the resistors and the power supplied by the battery.
- Do the same thing for figure 2.

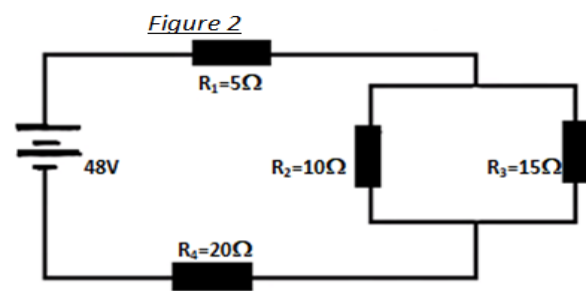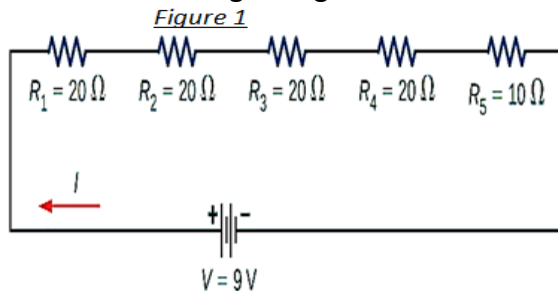**Exercise 10: Analysis of a parallel circuit**

Three resistors $R_1=1.00\Omega$, $R_2=2.00\Omega$, and $R_3=2.00\Omega$, are connected in parallel. The parallel connection is attached to a $V=3.00V$ voltage source.

- What is the equivalent resistance?
- Find the current supplied by the source to the parallel circuit.
- Calculate the currents in each resistor and show that these add together to equal the current output of the source.
- Calculate the power dissipated by each resistor.
- Find the power output of the source and show that it equals the total power dissipated by the resistors.

Exercise N° 11:


Consider the electrical circuit in the following figure, where the capacitors are initially completely discharged. We are given:

$E = 10\text{ V}$; $R_1 = 1\text{ k}\Omega$; $R_2 = 2\text{ k}\Omega$; $R_3 = 2.2\text{ k}\Omega$; $C_1 = 2.2\text{ }\mu\text{F}$; $C_2 = 3.3\text{ }\mu\text{F}$

1. Calculate the voltage across each of the capacitors, if each of them is charged to its final voltage. Calculate the charge carried by each capacitor.

2. Calculate the currents I_1 , I_2 , and I_3 in resistances R_1 , R_2 , and R_3 .

3. Calculate the energy stored by the system.

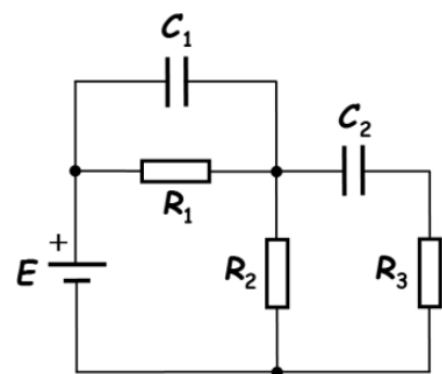**Exercise N°12:**

Consider the circuit in the following figure with:

$E = 10\text{ V}$; $E_1 = 5\text{ V}$; $E_2 = 3\text{ V}$; $E_3 = 6\text{ V}$; $R_1 = 1\text{ k}\Omega$; $R_2 = 2.2\text{ k}\Omega$; $R_3 = 3.3\text{ k}\Omega$;

1. Calculate the current intensity in each branch of the circuit.

2. Calculate the total power dissipated in the circuit.

