

Exam

Level: 1st Year

Material: Electricity


Date: Monday 13/01/2025

Duration: 2h

Exercise1: (7pts)

In the network shown in figure, the voltage source, with zero internal impedance, delivers an electromotive force of $e(t) = E\sqrt{2} \cos(\omega t)$ with $E = 1V$ and $\omega = 4 \text{ rad/s}$, $L=0.05 \text{ H}$, $R_1=R_2=2\Omega$ and $C_1=C_2=0.125 \text{ F}$.


- 1- Calculate the impedances of the reactive elements.
- 2- Calculate the complex admittance of the circuit (R_2, C_2) and the complex impedance of the circuit (R_1, C_1).
- 3- Calculate the equivalent complex admittance of the circuit, and determine the magnitude and phase of the equivalent admittance. Give details of the intermediate calculations.
- 4- Deduce the complex value of the current delivered by the source and its instantaneous expression.
- 5- Calculate the active, reactive, apparent power and the power factor for this circuit.

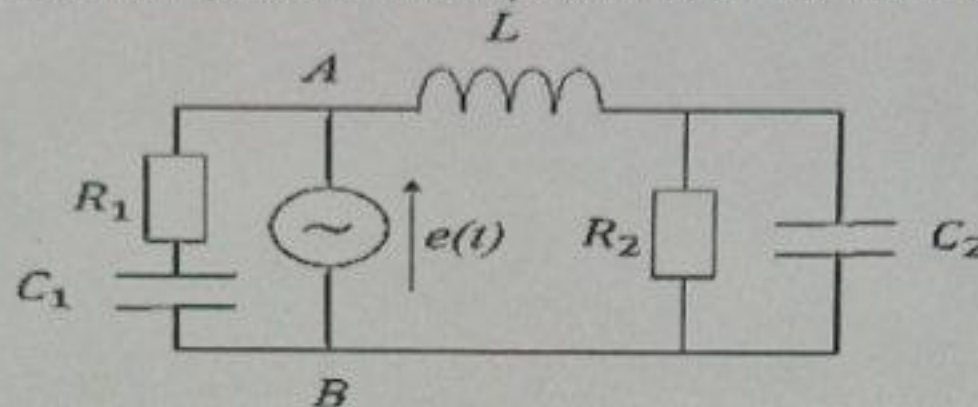

Exercise2: (8 pts)

- 1- Determine the Thevenin equivalent circuit (E_{th}, Z_{th}) corresponding to the active network below between points A and B.
- 2- A capacitor C is connected between A and B, such that $\frac{1}{C\omega} = 2\Omega$, determine the current flowing through this capacitor.
- 3- Deduce the Norton equivalent generator (I_N, Z_N).

Given: $L_1\omega = 16\Omega$, $L_2\omega = 4\Omega$, $L_3\omega = 5\Omega$, $R_1 = R_2 = 10\Omega$, $\underline{E}_1 = 10V \angle 0^\circ$, $\underline{E}_2 = 10V \angle 90^\circ$

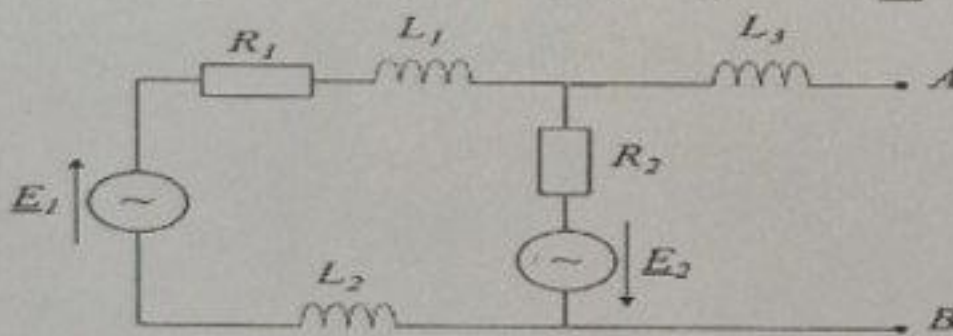

Exercise2: (5 pts)

- 1- Find out if there is a value of C to reach resonance at $f_0 = 2500/\pi \text{ Hz}$
 $R_1 = 8\Omega$, $R_2 = 8.34 \Omega$ and $Z_L = j8 [\Omega]$ (circuit in fig a)

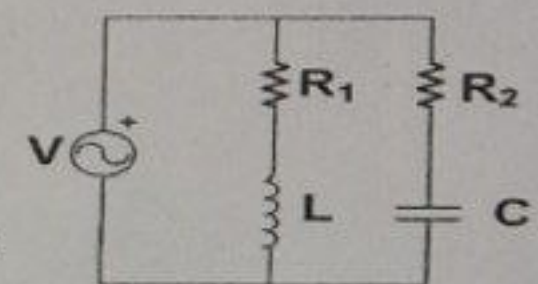


Fig a

- 2- Determine the resonance frequency of the circuit (see fig b) and calculate the value of current at the resonance. Given: $V_m = 20V$

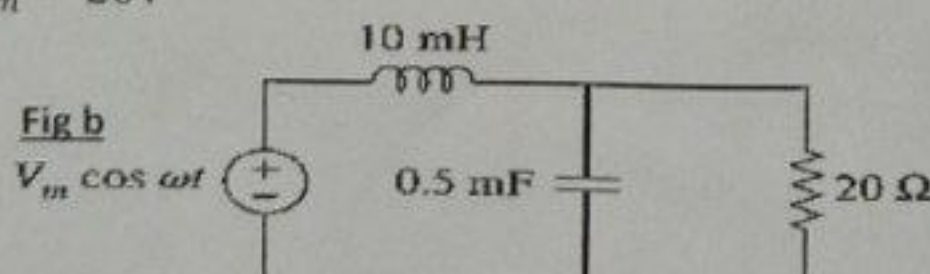


Fig b

$$2\pi f = \omega$$

$$8 = 0$$